

Table of Contents

Table of Contents.....	iii
Preface.....	viii
Getting Started.....	9
0.1 Breadboard	9
0.2 Power Supply.....	10
0.3 LEDs.....	10
0.4 Toggle Switches	11
0.5 Push Buttons	12
0.6 Debounced Push Buttons.....	12
0.7 Clock	13
0.8 Integrated Circuits	13
0.9 Circuit Construction	14
0.10 Materials and Parts	14
Chapter 1: Introductory Concepts.....	16
1.1 Introduction	16
1.2 Objectives	16
1.3 Discussion	16
1.3.1 Digital and Analog Circuits	16
1.3.2 Use of Binary Digital Ones and Zeros	18
1.3.3 Digital Circuits.....	19
1.4 Summary	21
1.5 Review Questions.....	21
Chapter 2: Number Systems and Codes.....	22
2.1 Introduction	22
2.2 Objectives	22
2.3 Discussion	22
2.3.1 The Binary Number System.....	23
2.3.2 Binary to Decimal Conversion.....	24
2.3.3 Decimal to Binary Conversion.....	24
2.3.4 The Hexadecimal Number System	25
2.3.5 The Octal Number System.....	26
2.3.6 Binary Coded Decimal System.....	26
2.3.7 ASCII Code	27
2.4 Summary	28
2.5 Review Questions.....	29
Chapter 3: Logic Gates and Boolean Algebra.....	30
3.1 Introduction	30
3.2 Objectives	30
3.3 Discussion	30
3.3.1 Boolean Variables.....	30
3.3.2 Truth Tables.....	30
3.3.3 The AND Operation.....	31
3.3.4 The OR Operation.....	32
3.3.5 The NOT Operation.....	32
3.3.6 Logic Equations	33
3.3.7 Logic Circuits	34
3.3.8 AND, OR and NOT Gates	34
3.3.9 NAND and NOR Gates.....	35

3.4	Summary	35
3.5	Review Questions	36
3.6	Lab Exercise 3.1: The NOT Gate (Inverter)	36
3.7	Lab Exercise 3.2: The And Gate	40
3.8	Lab Exercise 3.3: The OR Gate	41
3.9	Lab Exercise 3.4: The NAND Gate	41
3.10	Lab Exercise 3.5: The NOR Gate	42
3.11	Lab Exercise 3.6: Using the NAND Gate for Any Logic Function	43
3.12	Lab Exercise 3.7: Using the NOR Gate for Any Logic Function	44

Chapter 4: Combinational Logic Circuits..... **46**

4.1	Introduction	46
4.2	Objectives	46
4.3	Sum-Of-Products Form	46
4.4	Designing Combination Circuits	47
4.5	Boolean Simplification	48
4.6	DeMorgan's Theorem.....	49
4.7	The Karnaugh Map	50
4.8	Don't Cares.....	55
4.9	Product-Of-Sums Form	56
4.10	The Exclusive OR And Exclusive NOR Circuits	59
4.11	Summary	59
4.12	Review Questions	60
4.13	Lab Exercise 4.1: Minterm and Maxterm Truth Tables.....	61
4.14	Lab Exercise 4.2: Simplifying Logic Circuits	63
4.15	Lab Exercise 4.3: Decoders	65
4.16	Lab Exercise 4.4: Multiplexers.....	66
4.17	Lab Exercise 4.5: The XOR Circuit	67
4.18	Lab Exercise 4.6: The XNOR Circuit.....	68

Chapter 5: Latches and Flip-Flops..... **69**

5.1	Introduction	69
5.2	Objectives	69
5.3	Discussion	69
5.3.1	SR Latch	70
5.3.2	D Latch	71
5.3.3	SR Latch with Enable	72
5.3.4	D Latch with Enable	73
5.3.5	T Latch.....	73
5.3.6	JK Latch.....	74
5.3.7	Clock Signal.....	75
5.3.8	D Flip-Flop	76
5.3.9	JK Flip-Flop	77
5.3.10	Counting and Frequency Division	77
5.3.11	Monostable Multivibrators.....	78
5.4	Summary	78
5.5	Review Questions	78
5.6	Lab Exercise 5.1: SR Latches	79
5.7	Lab Exercise 5.2: The D Latch.....	81
5.8	Lab Exercise 5.3: The SR Latch with Enable	82
5.9	Lab Exercise 5.4: The D Latch with Enable	83
5.10	Lab Exercise 5.5: The D Flip-flop	84
5.11	Lab Exercise 5.6: The T Flip-flop	85
5.12	Lab Exercise 5.7: The J-K Flip-flop	86
5.13	Lab Exercise 5.8: The One-shot	88

Chapter 6: Digital Arithmetic.....	90
6.1 Introduction	90
6.2 Objectives	90
6.3 Discussion	90
6.3.1 Binary Addition	90
6.3.2 Signed Numbers.....	90
6.3.3 Binary Subtraction	91
6.3.4 Binary Multiplication.....	92
6.3.5 Binary Division.....	93
6.3.6 Hexadecimal Arithmetic	94
6.3.7 BCD Addition	94
6.3.8 The Half-adder	95
6.3.9 Full-adder.....	95
6.3.10 Parallel Binary Adder.....	96
6.3.11 BCD Adder	96
6.3.12 Binary Multipliers	97
6.4 Summary	97
6.5 Review Questions	97
6.6 Lab Exercise 6.1: Binary Adders	98
6.7 Lab Exercise 6.2: Parallel Binary Adder	99
6.8 Lab Exercise 6.3: The BCD Adder	101
6.9 Lab Exercise 6.4: The ALU	104
Chapter 7: Counters and Registers.....	106
7.1 Introduction	106
7.2 Objectives	106
7.3 Discussion	106
7.3.1 Ripple Counters	106
7.3.2 MOD Counters.....	107
7.3.3 Down Counters	108
7.3.4 Parallel Counters.....	108
7.3.5 Parallel UP/DOWN Counter	109
7.3.6 Presetable Counters.....	110
7.3.7 IC Binary UP/DOWN Counter	110
7.3.8 Counter Decoding	111
7.3.9 Shift Registers.....	111
7.3.10 Johnson Counter.....	112
7.3.11 Integrated Circuit Registers.....	113
7.4 Summary	115
7.5 Review Questions	115
7.6 Lab Exercise 7.1: UP/DOWN Counters	116
7.7 Lab Exercise 7.2: Synchronous Counters	117
7.8 Lab Exercise 7.3: IC Counters	118
7.9 Lab Exercise 7.4: Shift Registers.....	121
7.10 Lab Exercise 7.5: The 74LS165	123
7.11 Lab Exercise 7.6: The 74LS164	124
Chapter 8: Integrated Circuit Logic Families.....	125
8.1 Introduction	125
8.2 Objectives	125
8.3 Discussion	125
8.3.1 Terminology	125
8.3.2 TTL Logic Family	126
8.3.3 Standard TTL Logic Characteristics	128
8.3.4 TTL Loading Rules.....	129

8.3.5	Using Specification Sheets	129
8.3.6	Open Collector Outputs	131
8.3.7	Three-State Logic	133
8.3.8	Other TTL Families	134
8.3.9	The MOSFET	135
8.3.10	CMOS	136
8.3.11	Interfacing CMOS and TTL	137
8.3.12	ESD Control	138
8.4	Summary	138
8.5	Review Questions	139
8.6	Lab Exercise 8.1: TTL Loading Rules	139
8.7	Lab Exercise 8.2: Open-Collector Logic Gates	140
8.8	Lab Exercise 8.3: Three-State Logic	141
8.9	Lab Exercise 8.4: TTL and CMOS Interfacing	141
Chapter 9: Medium Scale Integration	143	
9.1	Introduction	143
9.2	Objectives	143
9.3	Discussion	143
9.3.1	Decoders	143
9.3.2	BCD-to-Decimal Decoder	143
9.3.3	BCD-to-Seven Segment Display Decoders	144
9.3.4	Common Displays	145
9.3.5	Encoders	146
9.4	Multiplexers	147
9.4.1	Demultiplexers	150
9.4.2	3-State Registers	151
9.5	Summary	152
9.6	Review Questions	152
9.7	Lab Exercise 9.1: Decoders	152
9.8	Lab Exercise 9.2	154
9.9	Lab Exercise 9.3: Encoders	155
9.10	Lab Exercise 9.4: Digital Multiplexers	156
9.11	Lab Exercise 9.5: Demultiplexers	157
Chapter 10: Data Conversion and Acquisition	159	
10.1	Introduction	159
10.2	Objectives	159
10.3	Discussion	159
10.3.1	D/A Conversion	159
10.3.2	D/A Specifications	162
10.3.3	D/A Applications	163
10.3.4	A/D Conversion	163
10.3.5	Successive Approximation A/D	164
10.3.6	Data Acquisition	165
10.3.7	Sample and Hold Circuits	166
10.3.8	Multiplexing	166
10.4	Summary	168
10.5	Review Questions	168
10.6	Lab Exercise 10.1: D/A Converters	169
10.7	Lab Exercise 10.2	170
10.8	Lab Exercise 10.3: The Analog Multiplexer	172
Chapter 11: Potpourri	173	
11.1	Introduction	173
11.2	Objectives	173

11.3	Discussion	173
11.3.1	The 555 Timer.....	173
11.3.2	Opto-Isolators	175
11.3.3	DIP Relays	175
11.3.4	Programmable Logic Devices	175
11.4	Summary	178
11.5	Review Questions	178
11.6	Lab Exercise 11.1: The 555 Timer	178
11.7	Lab Exercise 11.2: DIP Relays.....	180
11.8	Lab Exercise 11.3: The Opto-Isolator	182
Chapter 12: Microcomputer Concepts.....	183	
12.1	Introduction	183
12.1.1	Objectives	183
12.1.2	What Is A Microcomputer?.....	183
12.1.3	Organization of the Microcomputer	184
12.1.4	Interfacing	188
12.1.5	Parallel and Serial Data Transmission	188
12.1.6	Programming.....	190
12.1.7	Machine Language.....	192
12.1.8	Assembly Language.....	193
12.1.9	High Level Language.....	194
12.2	Summary	194
12.3	Review Questions	195
Appendix A: IC Pin-outs.....	196	
Appendix B: IC Chips Parts List.....	203	